

TRANSISTORS

Bipolar Junction Transistors (BJT) npn transistor

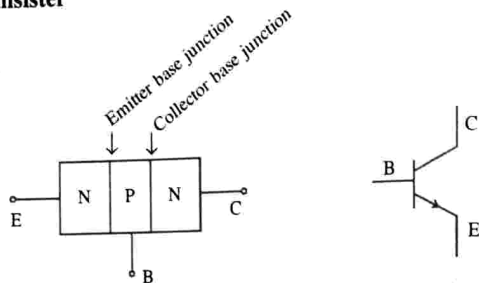


Fig. 2.1

pnp transistor

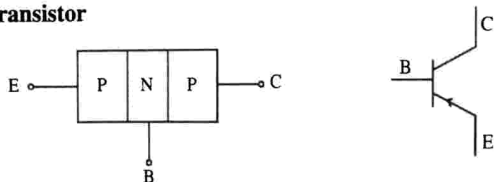


Fig. 2.2

Note : Emitter Base junction is always forward biased & collector base junction is always reverse biased.

Different transistor amplifier configurations

Transistor can be connected in three configurations

- Common Base (CB) – Base is common for both input & output circuits.

- Common Emitter (CE) – Emitter is common for both input & output circuits.
- Common Collector (CC) – Collector is common for both input & output circuits.

Common Base (CB) configuration

Here the Emitter base junction is forward biased by the battery V_{EE} and the collector Base junction is reverse biased by the battery V_{CC} .

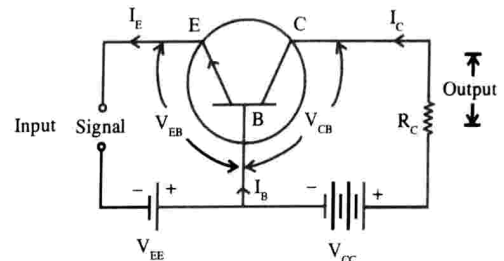


Fig. 2.3

Current amplification factor (α)

Ratio of change in collector current to the change in emitter current at constant collector base voltage V_{CB} is called current amplification factor.

$$\alpha_{ac} = \left. \frac{\Delta I_C}{\Delta I_E} \right|_{V_{CB} = \text{Constant}} \quad \alpha_{dc} = \frac{I_C}{I_E}$$

$I_C < I_E \therefore \alpha$ is always lesser than 1
 α lies from 0.9 to 0.99

Problems

1. Define α of a transistor and show that it is always less than unity. (CU Nov. 18)

Ans: $\alpha = \frac{\Delta I_C}{\Delta I_E}$, $I_C < I_E$, $\therefore \alpha$ is < 1

2. What is amplification factor? (CU Nov. 19)

Expression for collector current

Collector base junction is reverse biased. Due to this a very small reverse saturation current I_{CBO} (collector to base leakage current) flows across this junction.

$$\begin{aligned} \text{Total collector current } I_C &= \alpha I_E + I_{\text{leakage}} \\ &= \alpha I_E + I_{CBO} \end{aligned} \quad (1)$$

By KCL,

$$I_E = I_C + I_B$$

Substituting in ①

$$I_C = \alpha(I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$I_C(1 - \alpha) = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{I_{CBO}}{1 - \alpha} \quad (2)$$

Collector current can be controlled either by I_E or by I_B
[see equations (1) & (2)]


Problem

3. In a transistor if $I_C = 4.9\text{mA}$ and $I_E = 5\text{mA}$, Find the value of α .

$$\alpha = \frac{I_C}{I_E} = \frac{4.9}{5} = 0.98$$

Characteristics of Common Base Connection

Common-Base circuit

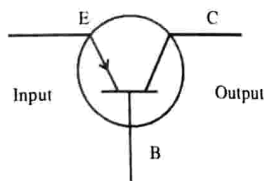

Common base configuration of pnp transistor

Fig. 2.4

Here the base terminal is common to both input and output terminals. The emitter terminal is taken as input and collector is taken as output terminal.

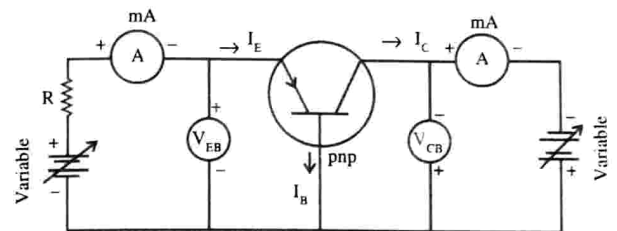


Fig. 2.5

Input characteristics – (V_{EB} versus I_E) and $V_{CB} = \text{constant}$

Output voltage V_{CB} is kept constant. For each value of input voltage V_{EB} , corresponding value of I_E is noted. Graph is plotted by taking V_{EB} along x-axis and I_E along y-axis.

The figure shows the input characteristics for different values of V_{CB} . In each case V_{CB} is kept constant.

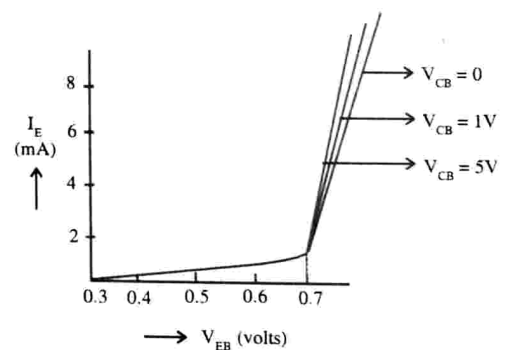


Fig. 2.6

$$\text{Input resistance } R_i = \left(\frac{\Delta V_{EB}}{\Delta I_E} \right)_{V_{CB}=\text{Constant}}$$

Output characteristics - (V_{CB} versus I_C) and $I_E = \text{constant}$

I_E is kept constant. V_{CB} is varied. Corresponding values of I_C are noted.

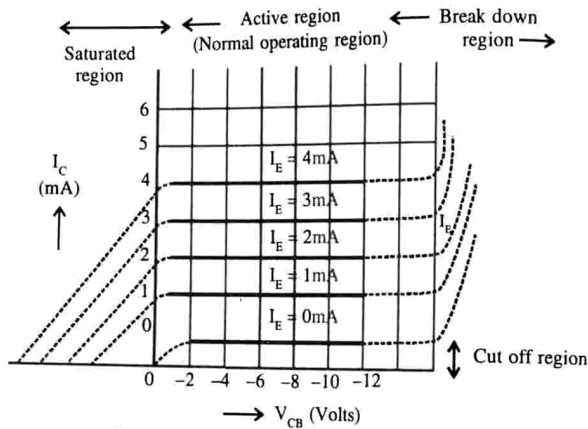


Fig. 2.7

Experiment is repeated for another value of I_E . Keeping I_E constant (say 2mA), V_{CB} is varied. Corresponding values of I_C are noted.

Even when V_{CB} is reduced to zero, I_C flows. This is due to the barrier voltage existing at the collector base junction.

If we increase V_{CB} , breakdown occurs at collector-Base junction.

Note : [Transistor is called a **current operating device**. This is because input current I_E controls output current I_C]

$$\text{Output resistance } R_o = \left(\frac{\Delta V_{CB}}{\Delta I_C} \right)_{I_E=\text{constant}}$$

Saturation region is the region located to the left of the line $V_{CB} = 0$ and above the output characteristics of emitter current $I_E = 0$. In this region, the collector current I_C increases sharply for a small change in V_{CB} .

Active region is the region located to the right of the line $V_{CB} = 0$ and above the emitter current $I_E = 0$. Here collector current I_C is constant ($I_C \approx I_E$).

Properties of C-B configuration

1. Voltage gain is very high
2. Current gain $\alpha = \frac{\Delta I_C}{\Delta I_E}$ is always less than 1.
3. Input resistance R_i is low.
4. Output resistance R_o is large.
5. Transistor in CB mode can be used as a constant current source.
6. Input and output voltages are in phase. So it can be used as a noninverting amplifier.

Problems

4. For the CB circuit shown in fig.2.8 determine I_C and V_{CB} . Transistor is made of Si.

Ans: For Si transistor

$$V_{BE} = 0.7V$$

Apply KVL to mesh ①

$$I_E R_E = V_{EE} - V_{BE}$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$= \frac{6 - 0.7}{1.2 \times 10^3} = \frac{5.3}{1.2 \times 10^3} = 4.42 \times 10^{-3} A$$

$$I_C \approx I_E = 4.42mA$$

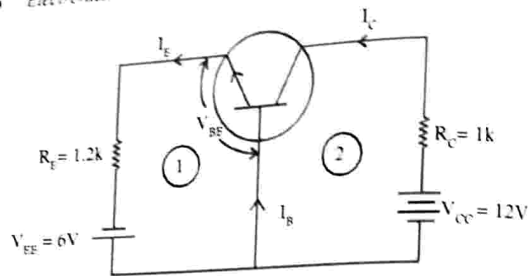


Fig. 2.8

Apply KVL to mesh ②

$$I_C R_C = V_{CC} - V_{CB}$$

$$\begin{aligned} V_{CB} &= V_{CC} - I_C R_C \\ &= 12 - 4.42 \times 10^{-3} \times 1 \times 10^3 \\ &= 7.58 \text{ V.} \end{aligned}$$

5. Draw the input and output characteristics of CB connection. What do you infer from these characteristics? (CU Nov. 19)

Common Emitter Configuration

Base current amplification factor (β):

The ratio of change in collector current (ΔI_C) to the change in base current (ΔI_B) is called base current amplification factor.

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

Common Emitter (CE) Characteristics CE circuit

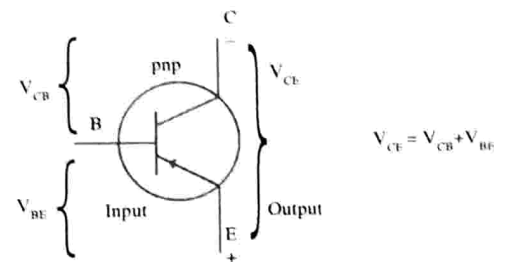


Fig. 2.9

Here the emitter terminal is common to both input as well as output. The base terminal is taken as input and collector terminal as output.

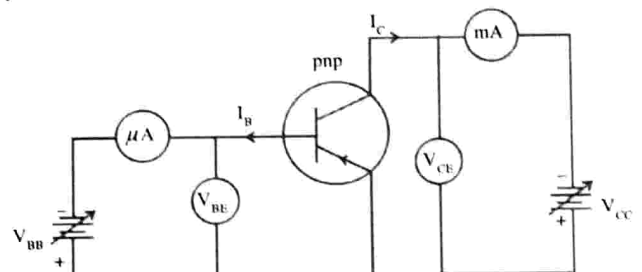


Fig. 2.10

Input characteristics – (V_{BE} Versus I_B) and $V_{CE} = \text{constant}$

V_{CE} is kept constant. V_{BE} is set and corresponding I_B levels are noted. V_{BE} is taken along X-axis and I_B is taken along Y-axis.

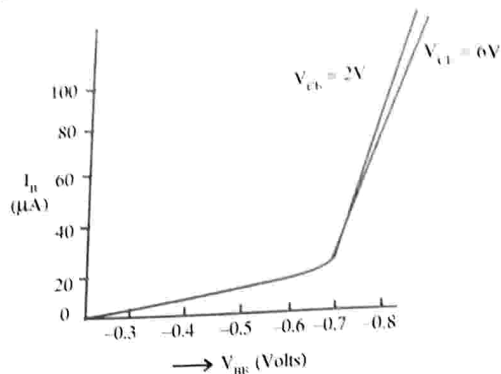


Fig. 2.11

$$\text{Input resistance, } R_i = \left[\frac{\Delta V_{BE}}{\Delta I_B} \right]_{V_{CE} = \text{constant}}$$

Output characteristics – (V_{CE} versus I_C) and $I_B = \text{constant}$

The output characteristics are drawn by noting output voltage V_{CE} and the collector current I_C keeping base current I_B constant.

In active region, collector junction is reverse biased and emitter junction is forward biased. In figure active region is the area to the right of ordinate $V_{CE} = \text{a few tenths of volt}$ and above $I_B = 0$.

When V_{CE} exceeds 0.7 V, the base-collector junction becomes reverse biased and the transistor goes into the active region. I_C increases very slightly as V_{CE} increases. This is due to widening of the base collector depletion region. This phenomenon is called **early effect**. In other words, the slope of the output characteristics is called the early effect.

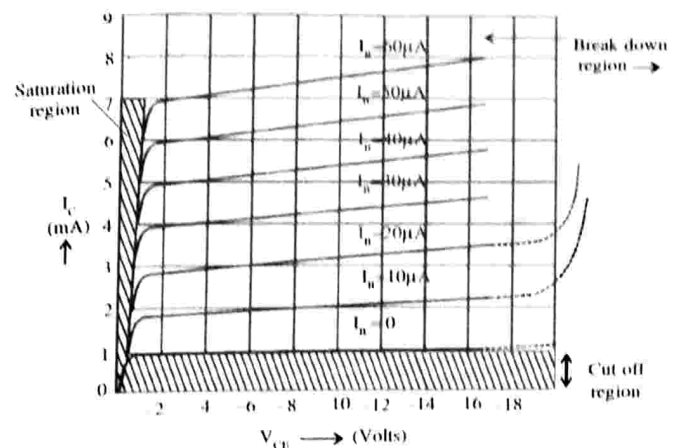


Fig. 2.12

When the characteristics are extended to the left of the current axis, they meet at a point on the horizontal axis.

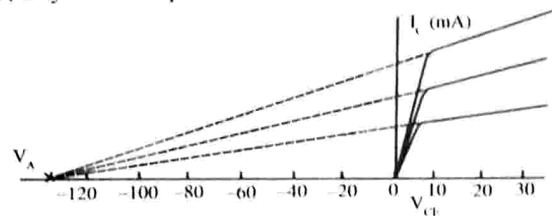


Fig. 2.13

The voltage at the point of intersection is around -100 V to -200 V. (in fig. 2.13, -120 V). This voltage V_A is known as **early voltage**.

A small collector current exists even when $I_B = 0$. This is called **leakage current**.

The collector current is zero, when the base current is zero. Under

this condition the transistor is in the **cut-off** state. The existing small collector current is called **collector cut off current**.

Properties of CE configuration

1. Voltage and current gains in CE mode are greater than 1
2. The input resistance is high. Output is also high.
3. Transistor in CE mode can be used as a voltage or power amplifier.
4. Input and output voltages are out of phase by 180° . So it can be used as an inverting amplifier with $A_v > 1$.

Problems

6. A transistor has an emitter current of 12mA and a collector current of 11.95mA. Find its base current.

$$\begin{aligned} \text{Ans: } I_E &= I_B + I_C \\ I_B &= I_E - I_C \\ &= 12 - 11.95 \\ &= 0.05\text{mA} \end{aligned}$$

7. Sketch the output characteristic of a common emitter configuration and discuss all the regions in the characteristic curve. (CU Nov. 20)
8. The most commonly used transistor arrangement is - configuration. (CU Nov. 20)

Ans: CE (Common Emitter)

Relation between α and β

(CU Nov. 17)

$$I_E = I_B + I_C \quad \dots (1)$$

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E \quad \dots (2)$$

Substituting (1) in (2)

$$\begin{aligned} I_C &= \alpha(I_B + I_C) \\ &= \alpha I_B + \alpha I_C \end{aligned}$$

$$I_C - \alpha I_C = \alpha I_B$$

$$I_C(1 - \alpha) = \alpha I_B$$

$$\frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

Problems

9. For a transistor the value of $\beta = 50$, then the value of $\alpha =$ ---

(CU Nov. 17)

Ans: 0.98.

10. For a transistor, the value of α is 0.9. Then the value of β is -

(CU Nov. 20)

Ans: 23

11. A transistor has $\alpha = 0.97$ and $I_B = 200 \mu\text{A}$. Calculate I_C , I_E and h_{FE} for the transistor.

$$(i) \quad I_C = \frac{\alpha I_B}{1 - \alpha} = \frac{0.97 \times 200 \times 10^{-6}}{1 - 0.97} = \mathbf{6.47\text{mA}}$$

$$(ii) \quad I_C = \alpha I_E$$

$$I_E = \frac{I_C}{\alpha} = \frac{6.47 \times 10^{-3}}{0.97} = \mathbf{6.67\text{mA}}$$

$$\begin{aligned} (iii) \quad h_{FE} = \beta &= \frac{\alpha}{1 - \alpha} = \frac{0.97}{1 - 0.97} \\ &= \frac{0.97}{0.03} = \mathbf{32}. \end{aligned}$$

12. In a common base connection $\alpha = 0.95$. The voltage drop across $2K\Omega$ resistance which is connected in the collector is 2V. Find the base current (KU May 16)

$$I_C = \frac{2V}{2K\Omega} = \frac{2}{2 \times 10^3} = 10^{-3} A = 1mA$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.95}{1-0.95} = \frac{0.95}{0.05} = 19$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{1 \times 10^{-3}}{19} = 0.053 \times 10^{-3} A$$

13. A transistor has measured currents of $I_C = 3mA$ and $I_E = 3.03 mA$. Calculate the new current levels when the transistor is replaced with a device that has $\beta = 75$. Assume that I_B remains constant.

$$\alpha = \frac{I_C}{I_E} = \frac{3}{3.03} = 0.99$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{1-0.99} = \frac{0.99}{0.01} = 99$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{3mA}{99} = 0.03 \times 10^{-3}$$

$$= 30\mu A$$

For new transistor

$$I_B = \frac{I_{C1}}{\beta_1}$$

$$30 \times 10^{-6} = \frac{I_{C1}}{75}$$

$$I_{C1} = 2250 \times 10^{-6} = 2.25mA$$

$$\beta_1 = \frac{\alpha_1}{1-\alpha_1}$$

$$75 = \frac{\alpha_1}{1-\alpha_1}$$

$$75 - 75\alpha_1 = \alpha_1$$

$$76\alpha_1 = 75$$

$$\alpha_1 = \frac{75}{76} = 0.987$$

$$\alpha_1 = \frac{I_{C1}}{I_{E1}}$$

$$0.987 = \frac{2.25}{I_{E1}}$$

$$I_{E1} = \frac{2.25}{0.987} = 2.28mA$$

14. Determine α and I_B for a transistor that has $I_C = 2.5mA$ and $I_E = 2.55mA$. Calculate β for the transistor.

$$\alpha = \frac{I_C}{I_E} = \frac{2.5}{2.55} = 0.98$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.5 \times 10^{-3}}{49} = 0.051 \times 10^{-3} \text{ mA} = 51 \mu\text{A}$$

15. A given transistor has a current gain $\beta = 50$. In common-base configuration, find the theoretical a.c. collector current flows when ac current of 2mA flows through the emitter. The collector potential is kept constant.

$$\alpha = \frac{\beta}{\beta + 1} = \frac{50}{51} = 0.98$$

$$\text{for ac } \alpha_{ac} = \frac{\Delta I_C}{\Delta I_E}$$

$$\Delta I_C = \alpha \Delta I_E = 0.98 \times 2 = 1.96 \text{ mA}$$

16. In a CE configuration, the collector supply voltage is 10V. The voltage drop across 500Ω connected in a collector circuit is 0.5 V. If $\alpha = 0.98$, find (i) the collector-emitter voltage and (ii) base current.

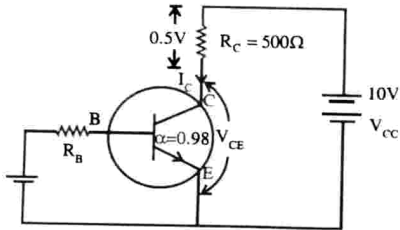


Fig. 2.14

- (i) In CE configuration

$$V_{CC} = V_{R_C} + V_{CE}$$

$$V_{CE} = V_{CC} - V_{R_C} = 10 - 0.5 = 9.5 \text{ V}$$

- (ii) Voltage drop across $R_C = I_C R_C = 0.5 \text{ V}$

$$I_C = \frac{0.5}{R_C} = \frac{0.5}{500} = 1 \text{ mA}$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{49} = 0.0204 \text{ mA}$$

17. What will be the base current of a transistor of $\alpha = 0.99$ and $I_E = 8 \text{ mA}$.

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E = 0.99 \times 8 \times 10^{-3} = 7.92 \text{ mA}$$

we have, $I_E = I_C + I_B$.

$$I_B = I_E - I_C = 8 - 7.92 = 0.08 \text{ mA}$$

18. The emitter current is 2mA in a CB configuration of a transistor. The emitter circuit is open. The collector leakage current $I_{CBO} = 0.050 \text{ mA}$. If $\alpha = 0.98$, find the total collector current.

$$\begin{aligned} I_C &= \alpha I_E + I_{CBO} \\ &= 0.98 \times 2 \times 10^{-3} + 0.050 \times 10^{-3} \\ &= 1.96 \text{ mA} + 0.050 \text{ mA} \\ &= 2 \text{ mA.} \end{aligned}$$

Common Collector Configuration

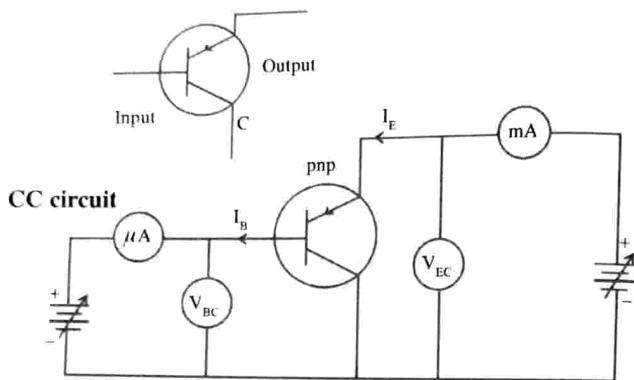


Fig. 2.15

Input characteristics

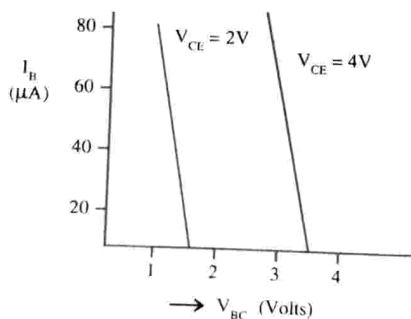


Fig. 2.16

Output characteristics

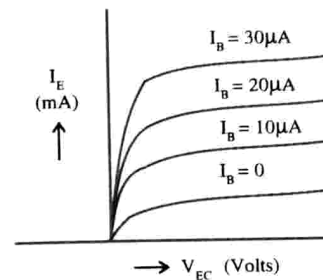


Fig. 2.17

Note: Current amplification in CB, CE and CC are α , β and γ

$$\alpha = \left(\frac{\Delta I_C}{\Delta I_E} \right)_{V_{CB} = \text{constant}}$$

$$\beta = \left(\frac{\Delta I_C}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$$

$$\gamma = \left(\frac{\Delta I_E}{\Delta I_B} \right)_{V_{CE} = \text{constant}}$$

Note : Relation between leakage current in CB, I_{CBO} and leakage current in CE, I_{CEO} is

$$I_{CEO} = (\beta + 1)I_{CBO}$$

Problems

19. $V_{cc} = 10V$. Transistor is connected in CE configuration. The voltage drop across 500Ω connected in collector circuit is $0.6V$. If $\alpha = 0.98$, find the collector-emitter voltage and base current.

Ans :

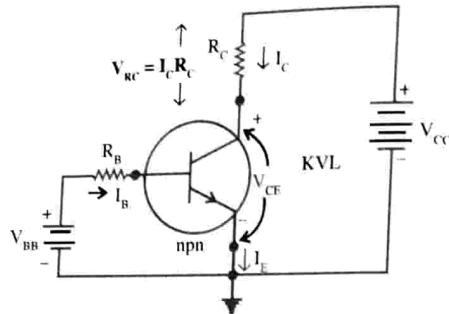


Fig. 2.18

In output circuit using KVL

$$I_C R_C = -V_{CE} + V_{CC}$$

$$V_{CE} = V_{CC} - I_C R_C \quad \because V_{RC} = I_C R_C = 0.6V$$

$$= 10 - 0.6$$

$$= 9.4V$$

$$I_C R_C = 0.6$$

$$I_C \times 500 = 0.6$$

$$I_C = \frac{0.6}{500} = 1.2 \text{ mA}$$

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.98}{1 - 0.98} = 49$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{1.2 \times 10^{-3}}{49} = 0.0245 \text{ mA}$$

20. In a transistor CE configuration, $V_{CC} = 12V$. Zero signal collector current is 1mA . What is the operating point if $R_C = 5K\Omega$

Ans : $I_C R_C = V_{CC} - V_{CE}$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 12 - (1 \times 10^{-3})(5 \times 10^3)$$

$$= 12 - 5 = 7V$$

\therefore Operating point (I_C, V_{CE}) is ($1\text{mA}, 7V$)

21. In a CB circuit, the emitter current is 1mA . The emitter circuit is open. The collector leakage current is $40\mu\text{A}$. Calculate the total collector current. α of the transistor = 0.98

Ans : Considering the leakage current I_{CBO}

In CB,

$$I_C = \alpha I_E + I_{CBO}$$

$$= 0.98 \times 1 \times 10^{-3} + 40 \times 10^{-6}$$

$$= 0.98\text{mA} + 40\mu\text{A}$$

$$= 1.020\text{mA}$$

22. In CE circuit, the collector current increases from 4mA to 4.02mA when the collector emitter voltage changes by $1V$. Find the output resistance.

Ans : $R_o = \left| \frac{\Delta V_{CE}}{\Delta I_C} \right|_{I_B = \text{constant}}$

$$= \frac{1}{0.02 \times 10^{-3}} = \frac{1000}{0.02} = 50000\Omega$$

23. The cut off current I_{CBO} for a transistor is $15\mu\text{A}$ at room temperature. $\beta = 50$. Calculate the collector current when base current is 0.2mA .

Ans : In CE, $I_C = \beta I_B + I_{CEO}$

$$I_{CEO} = I_{CBO} + \beta I_{CBO}$$

$$\begin{aligned} I_C &= \beta I_B + (\beta + 1) I_{CBO} \\ &= 50 \times 0.2 \times 10^{-3} + (50 + 1) 15 \times 10^{-6} \\ &= 10 \times 10^{-3} + 765 \times 10^{-6} \\ &= \mathbf{10.765 \text{ mA}} \end{aligned}$$

24. A transistor is connected in CE configuration in which collector supply is 10V and voltage drop across resistor $R_C = 800\Omega$ connected in the collector circuit is 0.5V. If $\alpha = 0.98$, determine
a) collector – emitter voltage b) base current

$$\begin{aligned} \text{Ans : } I_C R_C &= V_{CC} - V_{CE} & V_{CC} &= 10\text{V} \\ V_{CE} &= V_{CC} - I_C R_C & R_C &= 800\Omega \\ &= 10 - 0.5 = 9.5\text{V} & I_C R_C &= 0.5\text{V} \\ \beta &= \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha} & \alpha &= 0.98 \end{aligned}$$

$$\frac{I_C}{I_B} = \frac{0.5}{\frac{0.02}{0.98}} = \frac{0.98}{1 - 0.98} = \frac{0.98}{0.02}$$

$$\begin{aligned} I_B &= \frac{0.02}{0.98} \times \frac{0.5}{800} = \frac{0.01}{784} & \therefore I_C &= \frac{0.5}{800} = \frac{0.5}{800} \\ &= \mathbf{12\mu A} \end{aligned}$$

Comparison of transistor connections

Table 2.1

| Parameters | CB | CE | CC |
|---------------------------|--------------------------------|--------------------------------|--|
| R_i (input resistance) | Low ($\approx 100\Omega$) | Low ($\approx 750\Omega$) | Very high ($\approx 750\text{k}\Omega$) |
| R_o (output resistance) | $\approx 450\text{k}\Omega$ | $\approx 45\text{k}\Omega$ | $\approx 50\Omega$ |
| A_v (Voltage gain) | ≈ 150 | ≈ 500 | < 1 |
| Applications | for HF | for AF | for impedance matching |
| A_i (current gain) | < 1 | high | Appreciable |

25. The collector leakage current in a transistor is $250\mu\text{A}$ in CE configuration. If the same transistor is connected in CB configuration, find out the value of leakage current. β of the transistor is 100.

Ans :

Leakage current in CE, $I_{CEO} = 250\mu\text{A}$

$$\beta = 100$$

$$I_{CEO} = (\beta + 1) I_{CBO}$$

$$I_{CBO} = \frac{I_{CEO}}{\beta + 1}$$

$$= \frac{250 \times 10^{-6}}{100 + 1}$$

$$= \mathbf{2.5\mu A}$$

Note : $I_C = \beta I_B + I_{CEO}$

$$I_{CEO} = I_{CBO} + \beta I_{CBO} = (\beta + 1) I_{CBO}$$

Expression for voltage gain, Current gain and power gain of CE amplifier

Voltage gain (A_v)

It is the ratio of change in output voltage (ΔV_{CE}) to the change in input voltage (ΔV_{BE})

$$\begin{aligned}
 A_v &= \frac{\Delta V_{CE}}{\Delta V_{BE}} \\
 &= \frac{\text{change in output current} \times \text{effective load } (R_{AC})}{\text{change in input current} \times \text{input resistance}} \\
 &= \frac{\Delta I_C \cdot R_{AC}}{\Delta I_B \times R_i} \quad \text{where } R_{AC} = R_C // R_O \\
 &\quad R_O = \text{output resistance} \\
 &\quad R_i = \text{input resistance} \\
 &= \frac{\Delta I_C}{\Delta I_B} \cdot \frac{R_{AC}}{R_i} \\
 &= \beta \cdot \frac{R_{AC}}{R_i}
 \end{aligned}$$

For single stage amplifier, $R_{AC} = R_C$

For multistage $R_{AC} = \frac{R_C \times R_i}{R_C + R_i}$

Current gain (β)

It is the ratio of change in collector current (ΔI_C) to the change in base current (ΔI_B).

$$\text{Current gain } \beta = \frac{\Delta I_C}{\Delta I_B}$$

Input current becomes β times in the collector circuit.

Note : If β_1 and β_2 are individual stage gain of a two stage transistor circuit, then overall gain is $\beta = \beta_1 \beta_2$.

Power gain (A_p)

It is the ratio of output signal power to the input signal power.

$$\begin{aligned}
 A_p &= \frac{(\Delta I_C)^2 \times R_{AC}}{(\Delta I_B)^2 \times R_i} \\
 &= \left(\frac{\Delta I_C}{\Delta I_B} \right) \cdot \frac{\Delta I_C \times R_{AC}}{\Delta I_B \times R_i}
 \end{aligned}$$

$A_p = \text{current gain } (\beta) \times \text{voltage gain.}$

Cut off saturation points

Consider CE transistor circuit. Its output characteristics is as shown below.

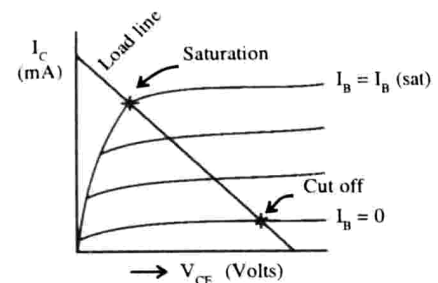


Fig. 2.19

Cut off

The point where the dc load line intersects the $I_B = 0$ curve.

Here small collector current exists.

At cut off, the base - emitter junction no longer remains forward biased and normal transistor action is lost.

Emitter diode and collector diode are OFF

Saturation

The point where the load line intersects the $I_B = I_{B(sat)}$ curve.

Here Base current is maximum.

At saturation, collector base junction no longer remains reverse biased and normal transistor action is lost.

Emitter diode and collector diode are connected as show in fig.

Active region

The region between cut off and saturation.

Here collector Base junction is reverse biased.

Base emitter junction is forward biased.

Transistor works normally.

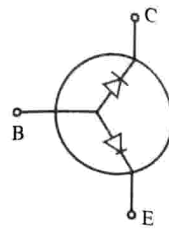


Fig. 2.20

Transistor Biasing

The proper flow of zero signal collector current and the maintainance of proper collector – emitter voltage during the passage of signal is called transistor biasing.

Purpose : to keep the base – emitter junction properly forward biased and collector base junction properly reverse biased.

Problem

26. Mention the essentials of a biasing circuit. (CU Nov. 19)

Different types of biasing

1. Base resistor method

(CU Nov. 17)

Base bias (or) fixed current bias using npn transistor

Here base Current remains constant. It is determined by V_{CC} (Supply voltage) and R_B (Base resistor). Since V_{CC} and R_B are constant quantities, I_B remains same.

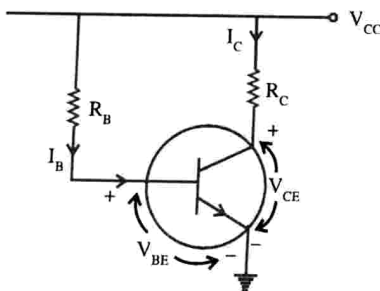


Fig. 2.21

Apply KVL to the input circuit

$$-I_B R_B = V_{BE} - V_{CC}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad \dots (1)$$

Here $V_{BE} = 0.7 \text{ V}$ for Si and 0.3 V for Ge transistors.

$$\beta = h_{FE} = \frac{I_C}{I_B} \quad \dots (2)$$

$$I_C = h_{FE} I_B \quad \dots (2)$$

Apply KVL to the output circuit

$$I_C R_C = -V_{CE} + V_{CC}$$

$$V_{CE} = V_{CC} - I_C R_C \quad \dots (3)$$

Substituting (2) in (3)

$$V_{CE} = V_{CC} - (h_{FE} I_B) R_C$$

If supply voltage V_{CC} , β and R_C are known base bias circuit can be easily constructed by using (1)

Problems

27 $R_B = 470 \text{ K}\Omega$, $R_C = 2 \text{ K}\Omega$, $V_{CC} = 12 \text{ V}$, β or $h_{FE} = 100$.

Find the values of I_B , I_C and V_{CE} . Given ($V_{BE} = 0.7 \text{ V}$).

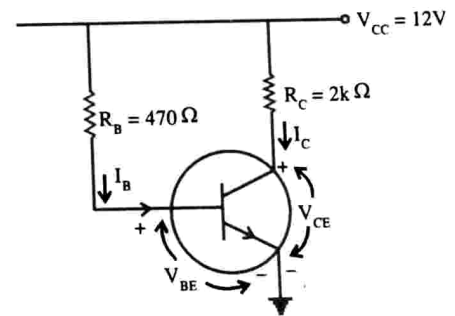


Fig. 2.22

Apply KVL to input

$$-I_B R_B = V_{BE} - V_{CC}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.7}{470} = \frac{11.3}{470} = 24 \mu\text{A}$$

$$h_{FE} = \beta = \frac{I_C}{I_B}$$

$$I_C = \beta \times I_B = 100 \times 24 \mu\text{A} \\ = 2.4 \text{ mA}$$

Apply KVL to output

$$I_C R_C = -V_{CE} + V_{CC}$$

$$V_{CE} = V_{CC} - I_C R_C \\ = 12 \text{ V} - (2.4 \text{ mA} \times 2 \text{ k}\Omega) \\ = 12 - 4.8 = 7.2 \text{ V}$$

28. From figure find $I_{C_{saturation}}$, I_C , V_C , V_E and V_{CE}

Note: Here emitter feedback is also included. R_E provides a form of -ve feedback that can be used to stabilize DC operating point)

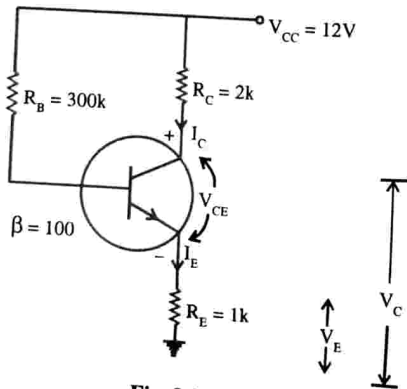


Fig. 2.23

$$I_{C_{saturation}} = \frac{V_{CC}}{R_E + R_C} = \frac{12}{1 + 2} = 4 \text{ mA}$$

$$\text{Actual } I_C = \frac{V_{CC}}{R_E + \frac{R_B}{\beta}} = \frac{12}{1 + \frac{300}{100}} = 3 \text{ mA}$$

Apply KVL to output circuit.

$$I_C R_C = V_{CC} - V_C$$

$$V_C = V_{CC} - I_C R_C = 12 - 3 \times 2 = 6 \text{ V}$$

$$V_E = I_E R_E \approx I_C R_E \\ = 3 \times 1 = 3 \text{ V}$$

$$V_{CE} = V_C - V_E = 6 - 3 = 3 \text{ V}$$

Base bias using a pnp transistor

Here polarities and directions of current are reversed compared to npn transistor base bias circuits.

Base Bias circuit design

Apply KVL to output circuit.

$$V_{CE} = V_{CC} - I_C R_C$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} \quad \dots (1)$$

Apply KVL to input circuit.

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} \quad \dots (2)$$

$$\text{Also } \beta = h_{FE} = \frac{I_C}{I_B}$$

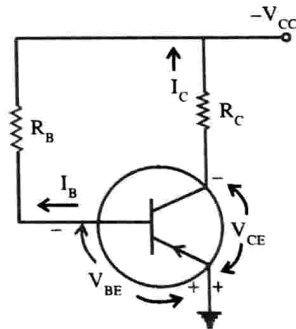


Fig. 2.24

$$\therefore I_B = \frac{I_C}{h_{FE}} \quad \dots (3)$$

29. Design a base circuit with $V_{CE} = 6V$ and $I_C = 5mA$. The supply voltage is $12V$. $\beta = h_{FE} = 100$

Ans:

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{12 - 6}{5 \times 10^{-3}}$$

$$= \frac{6}{5} \times 10^3 = 1.2 \times 10^3 = 1.2K\Omega$$

$$I_B = \frac{I_C}{\beta} = \frac{5 \times 10^{-3}}{100} = 50\mu A$$

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 - 0.7}{50 \times 10^{-6}} = \frac{11.3 \times 10^6}{50} = 0.226 \times 10^6$$

$$= 226K\Omega$$

30. Explain the difference between base bias and emitter bias circuits.

Ans:

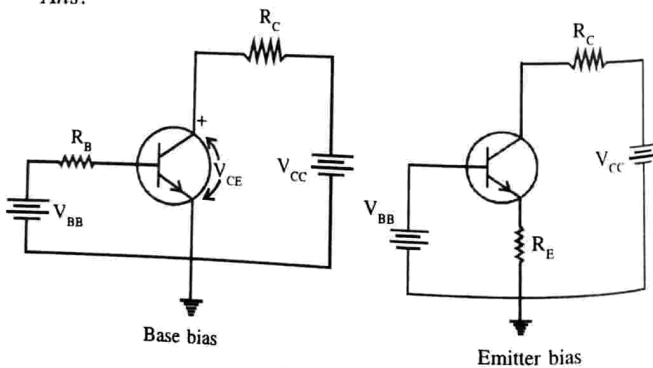


Fig. 2.26

Base Resistor moves from base circuit to the emitter circuit.

Base bias is used in digital circuits. Emitter bias used in amplifier circuits.

Advantages

1. Very simple (only one resistance R_B is required).
2. Calculations are simple.
3. Biasing conditions can easily be obtained.
4. No resistor is used across base emitter junction.

Disadvantage

1. Poor stabilization. [If β increases, I_C also increases ($\because I_B = \text{constant}$)]
2. Stability factor is very high.
3. There is a chance of thermal runaway.

Voltage divider bias method

It is the most stable bias circuit. Due to the change in β of the transistor or by change in temperature, the operating point may change. To compensate this variation, voltage divider bias is used. Here an additional resistance R_2 is connected between base and ground. The word 'voltage divider' comes from voltage divider formed by the resistors R_1 and R_2 .

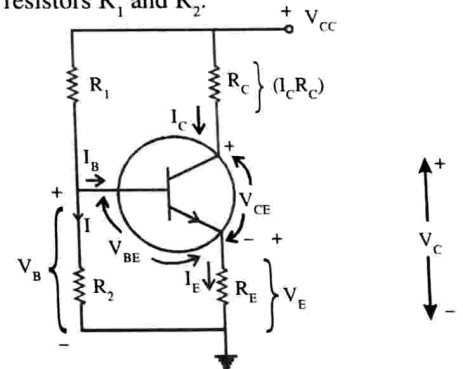


Fig. 2.27

According to the voltage divider circuit.

$$\begin{aligned} V_B &= IR_2 \\ &= \frac{V_{CC}}{R_1 + R_2} \cdot R_2 \\ V_{CC} \times \frac{R_2}{R_1 + R_2} &= V_B \end{aligned}$$

Apply KVL in lower mesh

$$\begin{aligned} -V_B + V_E + V_{BE} &= 0 \\ V_E &= V_B - V_{BE} \\ I_E R_E &= V_B - V_{BE} \\ I_E &= \frac{V_B - V_{BE}}{R_E} \end{aligned}$$

V_B , V_{BE} and R_E are constants.
 $\therefore I_E$ is constant.

$$I_E \approx I_C$$

$\therefore I_C$ is at constant level

From fig.

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

Substituting (4) in (5)

$$V_{CE} = V_{CC} - I_C R_C - V_E$$

$$\text{But } V_E = I_E R_E \approx I_C R_E$$

$$\therefore V_{CE} \approx V_{CC} - I_C R_C - I_C R_E$$

$$= V_{CC} - I_C (R_C + R_E)$$

Keeping I_C constant, V_{CE} remains constant.

Note: In any of the above equations β is not there. Voltage divider circuit does not depend on β .

31. Discuss the two biasing circuits used in CE amplifier configuration. Also explain how stabilization of operating point is achieved in each case and discuss the advantages of each circuit. (CU Nov. 20)

32. For the voltage divider circuit shown in figure find the emitter voltage V_E , collector voltage V_C and collector emitter voltage V_{CE} ($V_{BE} = 0.7V$).

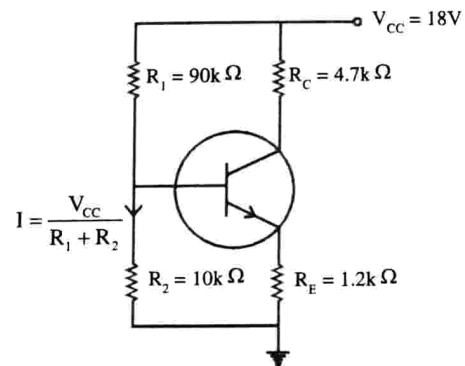


Fig. 2.28

$$V_B = \frac{V_{CC}}{R_1 + R_2} \times R_2 = V_{CC} \times \frac{R_2}{R_1 + R_2} \quad \dots (1)$$

$$= 18 \times \frac{10}{90 + 10} = \frac{180}{100} = 1.8V$$

$$V_E = V_B - V_{BE} = 1.8 - 0.7 = 1.1V \quad \dots (2)$$

$$I_E = \frac{V_B - V_{BE}}{R_E} = \frac{1.8 - 0.7}{1.2 \times 10^{-3}} = \frac{1.1}{1.2} \times 10^{-3} = 0.916mA$$

$$I_C \approx I_E = 0.916mA$$

$$\begin{aligned}
 V_C &= V_{CC} - I_C R_C \\
 &= 18 - 0.916 \times 10^{-3} \times 4.7 \times 10^3 \\
 &= 18 - 4.305 = 13.695 \text{ V} \\
 V_{CE} &= V_{CC} - I_C (R_C + R_E) \\
 &= 18 - 0.916 \times 10^{-3} (4.7 \times 10^3 + 1.2 \times 10^3) \\
 &= 18 - 5.4 = 12.6 \text{ V}
 \end{aligned}$$

Voltage-divider Bias circuit design

Rule: $I_2 = \frac{I_C}{10}$

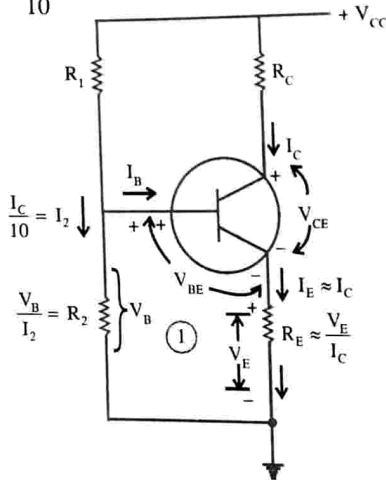


Fig. 2.29

Apply KVL to output

$$I_C R_C = -V_{CE} - V_E + V_{CC}$$

$$R_C = \frac{V_{CC} - V_{CE} - V_E}{I_C}$$

... (4)

In mesh (1)

$$-V_B + V_E + V_{BE} = 0$$

$$V_B = V_E + V_{BE}$$

$$(V_{BE} = 0.7 \text{ V})$$

... (5)

$$R_2 = \frac{V_B}{I_2} = \frac{V_B}{I_C/10} = \frac{10 V_B}{I_C}$$

Apply KVL,

$$-I_2 R_1 = V_B - V_{CC}$$

$$R_1 = \frac{V_{CC} - V_B}{I_2}$$

$$R_E = \frac{V_E}{I_C}$$

33. Design a voltage divider bias circuit in which $V_{CE} = V_E = 6\text{V}$ and $I_C = 1.5\text{ mA}$. The supply voltage is 24 V and the transistor $\beta = 80$

$$\text{Ans: } R_C = \frac{V_{CC} - V_{CE} - V_E}{I_C} = \frac{24 - 6 - 6}{1.5 \times 10^{-3}} = \frac{12 \times 10^3}{1.5}$$

$$= 8 \text{ k}\Omega$$

$$V_B = V_E + V_{BE} = 6 + 0.7 = 6.7$$

$$R_2 = \frac{V_B}{I_2} = \frac{6.7}{I_C/10} = \frac{67}{1.5 \times 10^{-3}} = \frac{67 \times 10^3}{1.5} = 44.67 \text{ k}\Omega$$

$$R_1 = \frac{V_{CC} - V_B}{I_2} = \frac{24 - 6.7}{I_C/10} = \frac{17.3}{1.5 \times 10^{-3}}$$

$$= \frac{173 \times 10^3}{1.5} = 115 \text{ k}\Omega$$

$$R_E = \frac{V_E}{I_C} = \frac{6}{1.5 \times 10^{-3}} = \frac{6 \times 10^3}{1.5} = 4 \text{ k}\Omega$$

34. If β of the transistor circuit shown in figure is 50, find the value of I_C using both α and β .

Ans :

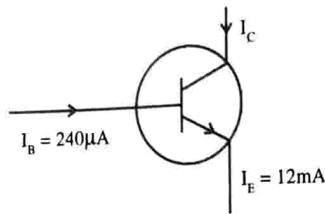


Fig. 2.30

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$50 = \frac{\alpha}{1 - \alpha}$$

$$50 - 50\alpha = \alpha$$

$$51\alpha = 50$$

$$\alpha = \frac{50}{51}$$

$$\alpha = \frac{I_C}{I_E}$$

$$\frac{50}{51} = \frac{I_C}{240 \times 10^{-6}}$$

$$I_C = \frac{50}{51} \times 240 \times 10^{-6}$$

$$\begin{aligned} &= 0.98 \times 240 \times 10^{-6} \\ &= 235.20 \times 10^{-6} \\ &= \mathbf{0.235 \text{ mA}} \end{aligned}$$

35. A CE connected transistor has $\beta = 50$ and $I_B = 20 \mu\text{A}$. Compute the values of I_C and I_E (CU Nov. 19)
36. A transistor has the following ratings $I_C (\text{max}) = 500 \text{ mA}$ and $\beta_{\text{max}} = 300$. Determine the maximum allowable value of I_B for the device (CU Nov. 19)
37. The α of an npn transistor is 0.98. The reverse saturation current I_{CBO} is $12.5 \mu\text{A}$. Determine the base current and collector current for an emitter current of 2 mA . (CU Nov. 11)

Ans:

Total collector current in CE,

$$I_C = \text{Total current in CB}$$

$$\begin{aligned} &= \alpha I_E + I_{CBO} \\ &= 0.98 \times 2 \times 10^{-3} + 12.5 \times 10^{-6} \\ &= 1.96 \times 10^{-3} + 0.0125 \times 10^{-3} \\ &= 1.9725 \times 10^{-3} \text{ A} \\ &= \mathbf{1.9725 \text{ mA}} \end{aligned}$$

$$\alpha = \frac{I_C}{I_E} = \frac{1.9725}{2} = 0.986$$

$$\begin{aligned} \beta &= \frac{\alpha}{1 - \alpha} = \frac{0.986}{1 - 0.986} = \frac{0.986}{0.014} \\ &= \mathbf{70} \end{aligned}$$

$$\beta = \frac{I_C}{I_B}$$

$$70 = \frac{1.9725 \times 10^{-3}}{I_B}$$

$$I_B = \frac{1.9725 \times 10^{-3}}{70}$$

$$= 28 \mu\text{A}$$

38. A transistor uses potential divider method of biasing. $R_1 = 50 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$ and $R_E = 1 \text{ k}\Omega$. If $V_{CC} = 12 \text{ V}$, find

(a) The value of I_C ; given $V_{BE} = 0.1 \text{ V}$.

(b) The value of I_C ; given $V_{BE} = 0.3 \text{ V}$.

Comment the result.

(CU Nov. 17)

Ans: (i) When $V_{BE} = 0.1 \text{ V}$, voltage across $R_2 = V_2$

$$= \frac{V_{CC} R_2}{R_1 + R_2}$$

$$= \frac{12 \times 10}{50 + 10} = \frac{120}{60} = 2 \text{ V}$$

$$\therefore I_C = \frac{V_2 - V_{BE}}{R_E}$$

$$= \frac{2 - 0.01}{1 \text{ k}\Omega} = 1.9 \text{ mA}$$

(ii) When $V_{BE} = 0.3 \text{ V}$, $I_C = 1.7 \text{ mA}$

Comment: I_C is almost independent of transistor parameter variations.

39. In figure collector current is 5 mA . Find collector-emitter voltage.

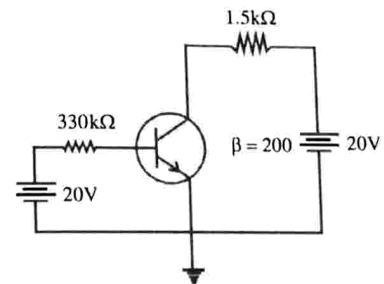


Fig. 2.31

$$\text{Ans: } V_{CE} = V_{CC} - I_C R_C$$

$$= 20 - (5 \times 10^{-3} \times 1.5 \times 10^3) = 20 - 7.5 = 12.5 \text{ V}$$

Comparison of bias circuits

Table 2.2

| Base bias | Collector to base bias | Voltage divider bias |
|--|--|--|
| 1. Only one resistance R_B is required | Only one resistance R_B is required | R_1, R_2, R_E form biasing |
| 2. Biasing conditions can be easily set and calculations are simple | Provides a -ve feedback which reduces the gain of the amplifier. | |
| 3. There is no loading of the source by the biasing circuit (\because no resistor is used across base-emitter junction) | | |
| 4. Provides poor stabilisation. If β increases due to transistor replacement I_C also increases by the same factor as I_B is constant. | Provides stabilisation. But it is not better. | Excellent stabilisation is provided by R_E (Not depending on β) |
| 5. There are chances for thermal run away | | |


40. Describe the various methods used for transistor biasing? State their advantages and disadvantages. (CU Nov. 19)

Single stage transistor amplifier circuit

Action

When only **one transistor** with associated circuitry is used for amplifying a weak signal, the circuit is called single stage transistor amplifier.

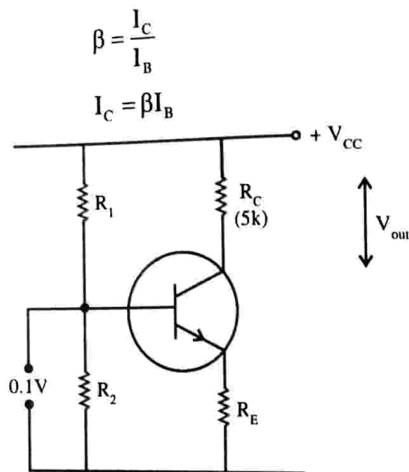When a weak a.c. signal (say 0.1v) is given to the base of a transistor, a small base current (a.c) starts flowing.



β is a large quantity

$\therefore I_C$ is large. When I_C flows through R_C

$$V_{out} = I_C R_C$$

The value of R_C is high.

$\therefore V_{out}$ is high

Thus a weak signal applied to base circuit appears in amplified form in the collector circuit.

In fig., suppose $V_{in} = 0.1V$

$$R_C = 5k\Omega$$

$$\beta = 100, I_B = 10\mu A$$

$$\therefore I_C = \beta I_B = 100 \times 10 \times 10^{-6} = 10^{-3} A$$

$$V_{out} = I_C R_C = 10^{-3} \times 5 \times 10^3 = 5V$$

$$\text{Voltage gain } A_v = \frac{V_{out}}{V_{in}} = \frac{5V}{0.1V} = 50$$


Problems

41. What do you understand by single stage transistor amplifier?
(CU Nov. 19)

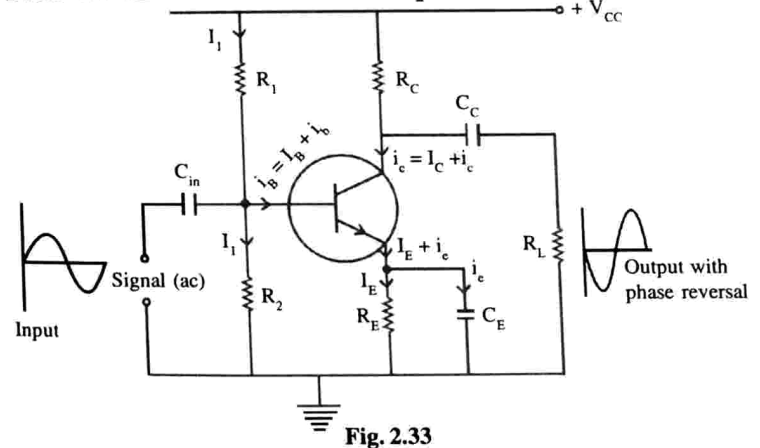42. Draw the circuit diagram of a single stage CE amplifier. Describe its working with necessary theory and explain frequency response curve.
(CU Nov. 20, CU Nov. 18)

Ans: Circuit diagram of CE amplifier using a transistor – Explanation – Frequency response curve by taking frequency along X-axis and gain in Y-axis – and its explanation – Lower cut of frequency, upper cut off frequency, Band width, 3db concept etc.

Practical circuit of transistor amplifier



R_1 , R_2 and R_E form the biasing and stabilisation circuit. This is for faithful amplification.

C_m is used to couple the signal to the base. It allows only a.c. signal to flow through it. i.e., signal source is isolated from R_2 . (If C_m is not used, a.c. signal comes across R_2 . This affects the biasing.)

C_E is connected in parallel with R_E . It provides an easy path to the amplified a.c. signal. (if C_E is not used, amplified a.c. signal will flow through R_E which produces a voltage drop across it. So output voltage will be reduced.)

C_C is the coupling capacitor. It is used to couple one stage of amplifier to the next. (If C_C is not used R_C will come parallel to R'_1 of the next stage (not in figure). So, for the next stage, instead of R'_1 , $R_C // R'_1$ will result. This will affect biasing condition of second stage.) C_C allows only a.c. signal to pass to the next stage.

Problem

43. What do you understand by single stage transistor amplifier?
(CU Nov. 19)

Currents

- (i) I_B : is the base current. This is d.c. It is due to biasing circuit.
- (ii) i_b : This flows when a.c. signal is applied.
Total Base Current $i_B = I_B + i_b$
- (i) I_C : is the collector current when no signal (a.c.) is applied. It is d.c.
(ii) i_c : when signal (a.c.) is applied i_c flows. It is a.c.
Total collector current $i_C = I_C + i_c$

Note : \therefore Zero signal collector current $I_C = \beta I_B$

When signal is applied $i_c = \beta i_b$.

- (i) I_E : When no signal is applied. It is d.c.
(ii) i_e : when signal (a.c.) applied i_e flows.
Total emitter current $i_E = I_E + i_e$.

Note : Apply KCL to the transistor

$$I_E = I_B + I_C$$

$$i_e = i_b + i_c$$

I_B and i_b are very small.

Load line analysis circuit

DC load line and Bias Point:

D.C load line is the line on the output characteristics of a transistor which gives the values of I_C and V_{CE} corresponding to zero signal.

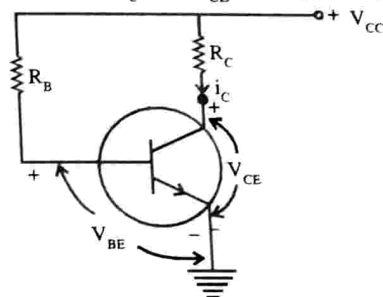


Fig. 2.34

Transistor functions linearly when it is made to operate in its active region.

Consider the output of common-emitter circuit as in figure 2.32 and apply KVL

$$I_C R_C = -V_{CE} + V_{CC}$$

dividing by R_C

$$I_C = \left(-\frac{1}{R_C} \right) V_{CE} + \frac{V_{CC}}{R_C} \quad \dots (1)$$

Eqn (1) is in the form of $y = mx + C$, which is the equation of a straight line.

Here slope of the line $m = -\frac{1}{R_C}$ and the constant $C = \frac{V_{CC}}{R_C}$ which is the intercept on Y-axis.

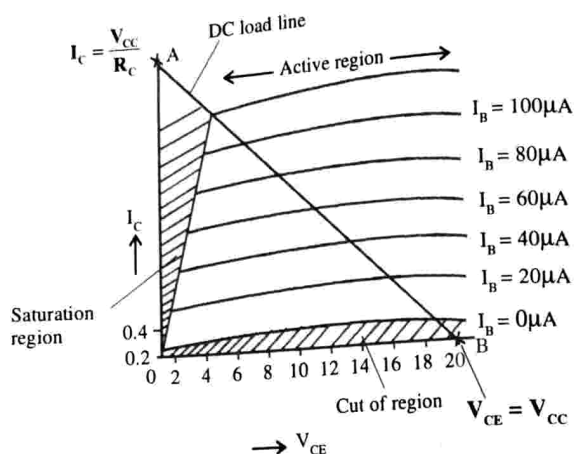


Fig. 2.35

In eqn (1) R_C and V_{CC} are constants. It is known as DC load line equation.

The two points required to draw the d.c. load line are found as follows

- i) When $V_{CE} = V_{CC}$, this gives the point **B** on X-axis. At this point the voltage drop across R_C is zero.

Substituting in (1)

$$I_C = \left(-\frac{1}{R_C} \right) V_{CC} + \frac{V_{CC}}{R_C} = 0$$

$$\therefore I_C R_C \text{ is zero.}$$

(or) when $I_C = 0$, $V_{CE} = V_{CC}$

- ii) When $V_{CE} = 0$,

$$(1) \rightarrow I_C = \frac{V_{CC}}{R_C}$$

This gives the point **A** on Y axis.

The straight line AB drawn through the above two points A and B is the **dc load line**. The inverse of slope of this line gives the resistance of the load.

The portion along the load line which includes all points between saturation and cut-off is known as the **Active region** of the operation of the transistor. Transistor is operated in this linear region. So the output is a linear reproduction of input.

Problem

44. How will you draw d.c. load line on the output characteristics of a transistor? What is its importance? (CU Nov. 19)

45. How load line is useful?

Ans: Load line represents effect of the load on collector current and V_{CE} . Load line contains every possible operating point. When R_B varies from zero to infinity, I_B varies. This makes I_C and V_{CE} to vary over the entire range. If we plot I_C and V_{CE} for every possible values of I_B , we get a load line.

Draw a DC load line for the given circuit

Apply KVL to output circuit

$$I_C R_C = -V_{CE} + V_{CC}$$

$$V_{CE} = V_{CC} - I_C R_C$$

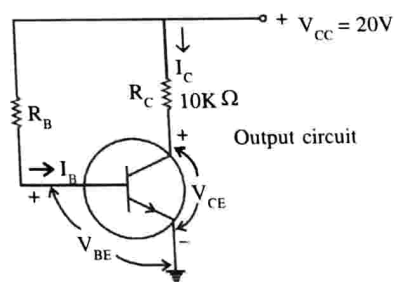


Fig. 2.36

When $I_C = 0$,

$$V_{CE} = V_{CC} = 20V.$$

The point A is fixed at this point on X-axis.

When $V_{CE} = 0$

$$0 = V_{CC} - I_C R_C$$

$$I_C R_C = V_{CC}$$

$$I_C = \frac{V_{CC}}{R_C}$$

$$= \frac{20}{10 \times 10^3}$$

$$= 2 \text{ mA.}$$

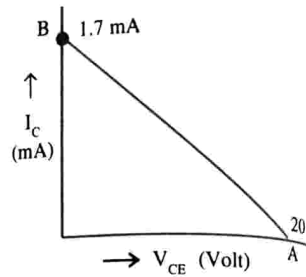


Fig. 2.37

The point B is fixed at this point on Y-axis. Drawing AB we get the DC load line.

DC Bias point (Q-point)

Apply KVL to the base circuit

$$-I_B R_B = V_{BE} - V_{CC}$$

$$I_B R_B = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

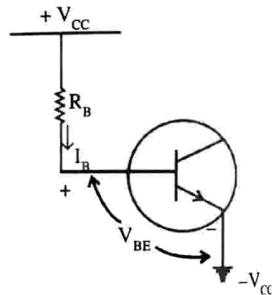


Fig. 2.38

For this value of I_B (which is a constant for a particular experiment) draw the output characteristic curve. The intersection of this curve and d.c. load line gives the operating point Q.

Q is called **quiescent point** (quiescent means quite or silent)

The **dc bias point** or **dc operating point** or **quiescent point** or **Q-point** is selected midway between the saturation and cut off where

to collector-to-emitter voltage V_{CE} is equal to nearly half of V_{CC} .

Selection of Q-point

If we fix Q point exactly at the half way along the load line, **faithful amplification** can be achieved. Now V_{CE} ranges from V_{CC} to zero when I_C goes from

zero to $\frac{V_{CC}}{R_C}$

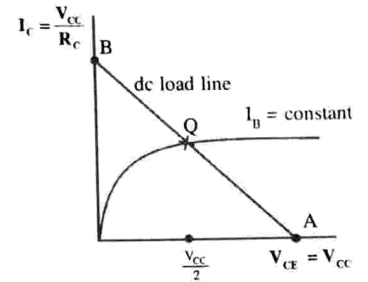


Fig. 2.39

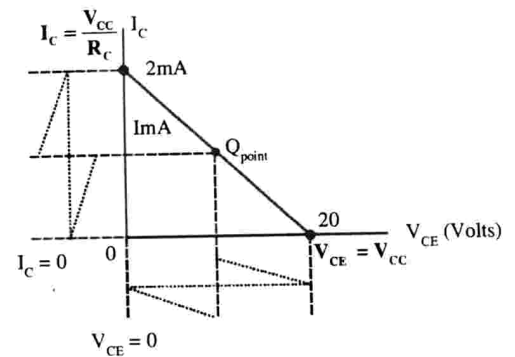


Fig. 2.40

Instead, the transistor is biased at $I_C = 0.5\text{mA}$ and $V_{CE} = 15V$

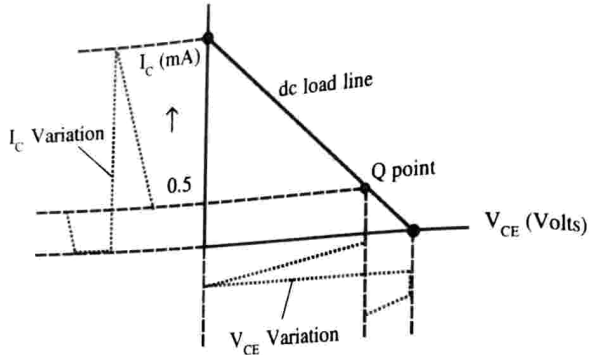


Fig. 2.41

Problems

Here the swing is not symmetrical above and below the bias point. When transistor is used as an amplifier, the transistor output voltage (V_{CE}) must swing up and down of the Q point by equal amounts. So

46. Write a short note on operating point (CU Nov. 19)

Q point must be at the centre of load line

47. $V_{CC} = 12V$, $R_C = 2k\Omega$ and $I_B = 30\mu A$. Find the Q point.

Ans: $V_{CE} = V_{CC} - I_C R_C$

When $I_C = 0$, $V_{CE} = 12V$

When $V_{CE} = 0$, $0 = 12 - I_C \times 2 \times 10^3$

$$I_C = \frac{12}{2 \times 10^3} = 6mA$$

So Q point will be at (12V, 6mA).

Note: Here the maximum symmetrical output voltage swing will

be $I_C = \frac{6}{2} = 3mA$ and $V_{CE} = \frac{12}{2} = 6V$ and $\Delta V_{CE} = \pm 9V$

48. Calculate the saturation current and cut-off voltage from the fig. given. Draw dc load line.

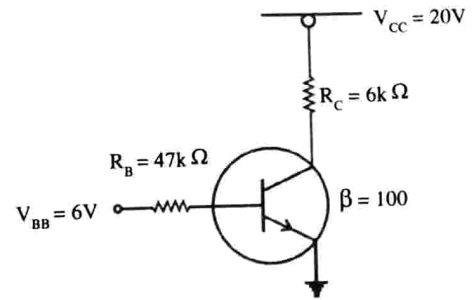


Fig. 2.42

Ans: $I_{C(saturation)} = \frac{V_{CC}}{R_C} = \frac{12V}{6k\Omega} = 2mA$

Cut off voltage, $V_{CE(cut\ off)} = V_{CC} = 12V$

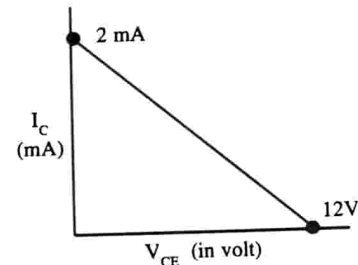


Fig. 2.43

49. Draw the dc load line. Find the dc working point (Q-point). $\beta = 100$. Neglect V_{BE} .

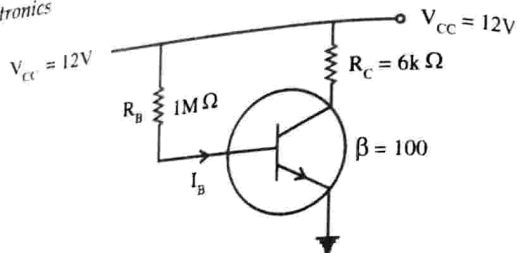


Fig. 2.44

$$\text{Ans: } I_{C(\text{saturation})} = \frac{V_{CC}}{R_C} = \frac{12}{6 \times 10^3} = 2\text{mA}$$

Cut off voltage $V_{CE(\text{cut off})} = V_{CC} = 12\text{V}$

DC load line is drawn

Apply KVL to the input circuit

$$-I_B R_B = V_{BE} - V_{CC}$$

$$V_{CC} = I_B R_B + V_{BE} \quad [V_{BE} \approx 0.7 \text{ neglected}]$$

$$I_B R_B = V_{CC}$$

$$I_B = \frac{V_{CC}}{R_B} = \frac{12}{1 \times 10^6} = 12\mu\text{A}$$

$$I_C = \beta I_B = 100 \times 12 \times 10^{-6} = 1.2\text{mA}$$

Apply KVL to the output circuit

$$I_C R_C = -V_{CE} + V_{CC}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 12 - 1.2 \times 10^{-3} \times 6 \times 10^3$$

$$= 12 - 7.2 = 4.8\text{V}$$

∴ Q point is (4.8V, 1.2mA)

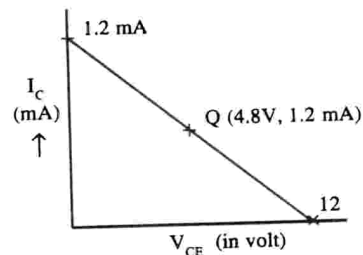


Fig. 2.45

50. A base bias circuit has $V_{CC} = 24\text{V}$, $R_B = 390\text{k}\Omega$, $R_C = 3.3\text{k}\Omega$ and $V_{CE} = 10\text{V}$. Calculate the transistor h_{FE} (or) β value.

Ans :

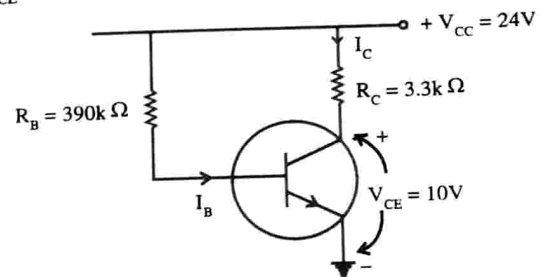


Fig. 2.46

$$\beta = \frac{I_C}{I_B}$$

... (1)

Apply KVL to output ckt.

$$I_C R_C = -V_{CE} + V_{CC}$$

$$= -10 + 24 = 14$$

$$I_C \times 3.3 \times 10^3 = 14$$

$$I_C = \frac{14}{3.3 \times 10^3} = 4.24 \times 10^{-3} \text{A} = 4.24\text{mA}$$

Apply KVL to input ckt.

$$-I_B R_B = V_{BE} - V_{CC}$$

$$I_B R_B = V_{CC} - V_{BE}$$

$$= 24 - 0.7 = 23.3\text{V}$$

$$I_B = \frac{23.3}{390 \times 10^3} = 0.0000597\text{A} = 59.7\mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = \frac{4.24 \times 10^{-3}}{59.7 \times 10^{-6}} = 0.0710 \times 10^3 = 71$$

Note: **Biasing helps** in setting a fixed level of current with a desired fixed voltage drop across the device.

Operating point is a fixed point on the output characteristics. It is specified by voltage & current values.

If voltage divider bias is taken $I_C = \frac{V_{CC}}{R_C + R_E}$ and $V_{CE} = V_{CC}$ are taken as two points.

51. How location of *Q* point is affected by changing current gain in a base bias circuit?

Ans: When current gain changes, I_B has no change. But I_C changes. When I_C changes V_{CE} changes. This shifts the *Q* point. If changes in current gain becomes much larger, the operating point shifts in to cut off or saturation region. Now amplifying circuit becomes useless. This is due to the loss of current gain outside the active region.

a.c. load line

a.c. equivalent circuits:

Capacitors behave as short-circuits to a.c. signals. So in a transistor circuit all capacitors are replaced with short circuits. Power supplies (including V_{CC}) are also behave as a.c. short circuits. (Because d.c. supply voltage is not affected by a.c. signals). So a.c. equivalent circuit of transistor amplifier can be drawn as

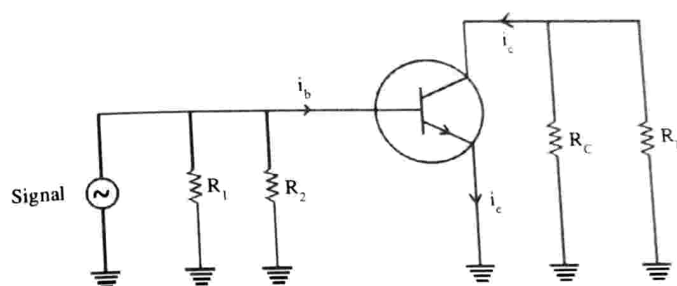


Fig. 2.47

When there is no input signal, the transistor voltage and current conditions are same as that of *Q* point on the d.c. load line. But when a.c. signal is applied, transistor voltage and current levels will change. They vary above and below *Q*-point. But *Q* point is common to both a.c. and d.c. load lines.

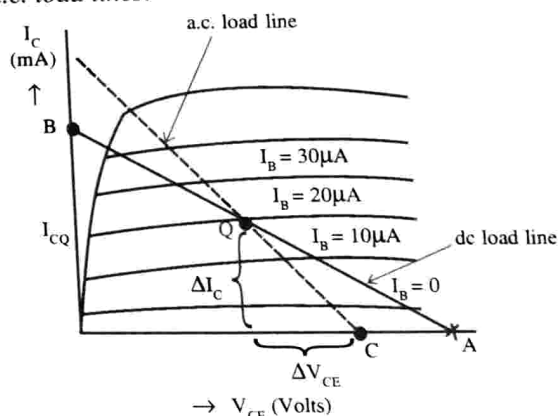


Fig. 2.48

Starting from *Q* point, another point is found on the a.c. load line by taking a convenient collector current change ($\Delta I_C = I_{CQ}$ in figure 2.48) and calculate corresponding change in collector emitter voltage (ΔV_{CE}).

For example : Let $V_{CC} = 20V$, $R_1 = 18k\Omega$, $R_2 = 8.2k\Omega$, $R_C = 2.2k\Omega$, $V_{BE} = 0.7V$.

Draw d.c. load line through A and B.

$$\text{Voltage across } R_2 \} V_B = \frac{V_{CC} \times R_2}{R_1 + R_2} = \frac{20 \times 8.2}{18 + 8.2} = 6.3V$$

$$\text{Voltage across } R_E \} V_E = V_B - V_{BE} = 6.3 - 0.7 = 5.6V$$

$$I_C = I_E = \frac{V_E}{R_E} = \frac{5.6}{2.7 \times 10^3} = 2.07mA.$$

Mark the Q point on the d.c. load line at $I_C = 2.07mA = I_{CQ}$.

To draw a.c. load line

Put $R_L = 0$

When I_C changes by $\Delta I_C = 2.07mA$

$$\Delta V_{CE} = \Delta I_C \times R_C = 2.07mA \times 2.2k\Omega = 4.55V.$$

Plot point C at $\Delta I_C = 2.07mA$ & $\Delta V_{CE} = 4.55V$ from the Q - point. Then draw a.c. load line through points C and Q. (see figure 2.48).

52. The point of intersection of DC and AC load line is
(CU Nov. 18)

Ans: Q - point

53. Draw the a.c. equivalent circuit of a single stage transistor amplifier circuit
(CU Nov. 20)

54. Determine the Q point of the transistor circuit shown in fig.2.49. Also draw the d.c. load line. Given

$$R_C = 1k\Omega, R_B = 47k\Omega,$$

$$R_E = 4.7k\Omega, V_{CC} = 10V, \beta = 100$$

$$\text{and } V_{BE} = 0.7V.$$

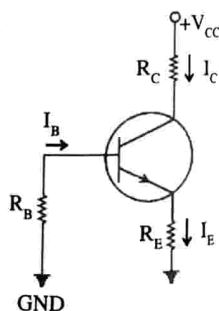


Fig. 2.49

Ans:

Hints : Find (i) Cut off voltage
(ii) Saturation current

- Draw the graph
- Find the operating point
- Mark the point in the graph.

Exercises

1. How are the two transistor junctions biased for a transistor operation?
2. n-p-n transistor is preferred over pnp transistor. Why?
3. Distinguish between α_{dc} and α_{ac} .
4. Distinguish between β_{dc} and β_{ac} .
5. Why base region of a transistor is narrow and lightly doped.
6. Bring out the relation between α and β of a transistor.
7. Explain the temperature dependance on current gain.

Ans: When temperature increases collector current increases. Therefore current gain increases.

8. What are the different types of transistor configurations? Draw circuit diagram of each type using NPN transistor. Explain each.
9. Sketch the input and output characteristics of NPN transistor in CE configuration.
10. Explain biasing of a transistor.
11. Explain the source of the leakage current in a transistor.
12. Explain the active, saturation and cut-off regions of a transistor.
13. Transistor means 'Transfer of Resistance'. Explain this statement.
14. Describe the action of pnp transistor
15. Describe the action of npn transistor
16. Explain leakage current in a transistor